34041 - Industrial Electronics

1. Power Devices And Trigger Circuits

Part - A

- 1. Draw the symbol of (i) GTO (ii) MOSFET.
- 2. Mention the isolation devices.
- 3. Draw the symbol of IGBT and MOSFET.
- 4. Mention the types of triggering of SCR.
- 5. What is GTO? Draw the symbol.

Part - B

- 1. Compare power MOSFET and power IGBT.
- 2. Explain AC gate triggering.
- 3. Write short notes on pulse transformer.
- 4. What is opto-coupler? State its functions.
- Compare power MOSFET with power transistor.

Part - C

- 1. Explain the working principle and VI characteristics of MOSFET with neat diagram. State its applications.
- 2. Explain the working principle of synchronized UJT triggering circuit with neat diagram and waveform.
- 3. Explain the working principle and VI characteristics of IGBT with neat diagram.
- 4. Explain the working principle of resistance capacitance firing circuit with neat diagram and waveforms.

2. Converters And Choppers

Part - A

- 1. Define converter and state its uses.
- 2. What is meant by chopper?
- 3. What is meant by forced commutation?
- 4. What is meant by natural commutation?
- State the applications of chopper.

Part - B

- 1. List the types of forced commutation.
- 2. State the importance of flywheel diode.
- 3. Draw the circuit diagram of single phase fully controlled bridge converter with RL load.
- 4. What is the purpose of using fly wheel diode in converter circuit?
- 5. What is forced commutation? List the types.

Part - C

- 1. Explain the working principle of single phase fully controlled bridge converter with R and RL loads with neat diagrams.
- 2. Explain the operation of Jones chopper with neat diagrams.
- Explain the working of DC chopper with diagrams.
- 4. Explain the working principle of single phase half controlled bridge converter with R and RL load with diagrams.
- 5. Draw and explain the working principle of AC chopper with diagrams.

3. Inverters And Applications

Part - A

- 1. Define inverters and mention its uses.
- 2. Define battery bank and mention its types.
- 3. What is SMPS? Mention its types.
- 4. List the methods of obtaining sine wave output from the inverter.
- 5. State the different methods to control the O/P voltage of inverter.

Part - B

1. List any three applications of SMPS.

Dept of ECE Page 1

34041 - Industrial Electronics

- 2. List the advantages and disadvantages of SMPS.
- 3. Compare online UPS with offline UPS.

Part - C

- With neat diagram explain the operation of bridge inverter with RL load.
- 2. Explain the two types of UPS with block diagram.
- 3. Explain the working principle of single phase inverter with waveforms and circuit diagram.
- 4. Draw the block diagram of SMPS and explain it. State its applications.
- 5. Explain the working principle of McMurray inverter with neat diagrams and state its advantages.
- 6. Draw the block diagram of SMPS and explain its functions. State its advantages.

4. Programmable Logic Controller

Part - A

- 1. Mention the various types of arithmetic operations performed in PLC.
- 2. State any four advantages of PLC.

Part - B

- 1. State the advantages of PLC.
- 2. What are the programming languages used in PLC?
- 3. Draw the symbol for the following items in ladder diagram:
 - (i) Normally opened contact (ii) Normally closed contact (iii) Output loads.
- 4. What is the function of I/P module used in PLC? List the I/P devices.
- 5. Draw the ladder diagram for the following gates: (i) OR gate (ii) AND gate (iii) Ex-OR gate

Part - C

- 1. Explain the various input and output modules used in PLC.
- 2. Draw and explain the ladder logic diagram of star delta starter.
- 3. Draw the block diagram of PLC and explain each block.
- 4. Draw the ladder diagram of conveyor control and explain.

5. Distributed Control Systems

Part - A

- 1. Specify the basic components of LCU.
- 2. What is DCS?

Part - B

- 1. State the features of DCS.
- 2. What is the function of LCU in distributed control system?
- 3. What is LCU? State its functions.

Part - C

- 1. Write notes on: (i) Plant display (ii) Area display.
- 2. Draw the architecture of hybrid system and explain it.
- 3. Draw and explain the architecture of distributed control system.
- Explain the features and advantages of DCS.

Dept of ECE Page 2